

ASSIGNMENT 1

CIRCUIT DESIGN HOME AUTOMATION SYSTEM IN TINKERCAD

CIRCUIT DIAGRAM

